



North South University

Department of Electrical & Computer Engineering

Lab Report

Experiment No: 04
Experiment Title: Design of a 3-bit Binary Up-Down counter
Course Code: CSE332L
Section: 07
Course Name: Computer Organization & Architecture Lab
Lab Group #: 02
Written By: Md. Nifat Hossain (2212923042)
Date of Experiment: 27.02.2025
Date of Submission: 13.03.2025

Group Members ID:	Group Members Name:
Md. Nifat Hossain	2212923042
Sudipto Roy	2222756042
Md. Muntasir Abid	2212773042
Mohammad Abdul Mannan Sami	2131206042

Objective:

- ① To build and understand the behaviour of an up-down counter.

Equipments List:

- Trainer Board
- IC 7404 (Not Gate), IC 7408 (AND Gate), IC 7432 (OR Gate)
IC 7486 (XOR gate), IC 7474 (D-flipflop)
- wires
- Power supply.

Block Diagram:

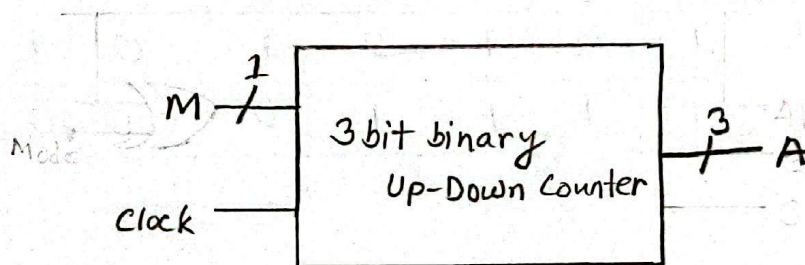


Fig: Block Diagram of 3-bit Up-Down Counter

Objective:

- ① To build and understand the behaviour of an up-down counter.

Equipments List:

- Trainer Board
- IC 7404 (Not Gate), IC 7408 (AND Gate), IC 7432 (OR Gate)
IC 7486 (XOR gate), IC 7474 (D-flipflop)
- wires
- Power supply.

Block Diagram:

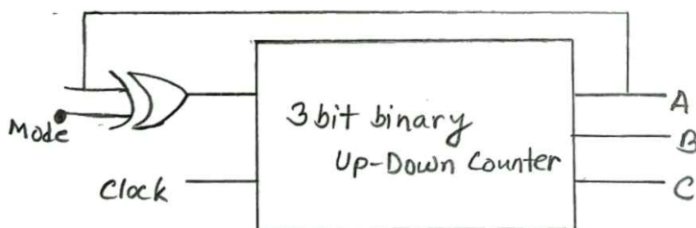


Fig: Block Diagram of 3 bit Up-Down Counter

Truth table :

M	Q_C	Q_B	Q_A	Q_C^+	Q_B^+	Q_A^+	T_C	T_B	T_A
0	0	0	0	0	0	1	0	0	1
0	0	0	1	0	1	0	0	1	1
0	0	1	0	0	1	1	0	0	1
0	0	1	1	1	0	0	1	1	1
0	1	0	0	1	0	1	0	0	1
0	1	0	1	1	1	0	0	1	1
0	1	1	0	1	1	1	0	0	1
0	1	1	1	0	0	0	1	1	1
1	0	0	0	1	1	1	1	1	1
1	0	0	1	0	0	0	0	0	1
1	0	1	0	0	0	1	0	1	1
1	0	1	1	0	1	0	0	0	1
1	1	0	0	0	1	1	1	1	1
1	1	0	1	1	0	0	0	0	1
1	1	1	0	1	0	1	0	1	1
1	1	1	1	1	1	0	0	0	1

K-Map:


	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	1	0	0	1
10	1	0	0	1

$$T_B = M\bar{Q}_B + \bar{M}Q_B$$

$$= M \oplus Q_B$$

	00	01	11	10
00	0	0	1	0
01	0	0	1	0
11	1	0	0	0
10	1	0	0	0

$$T_C = \bar{M}Q_CQ_B + M\bar{Q}_B\bar{Q}_C$$

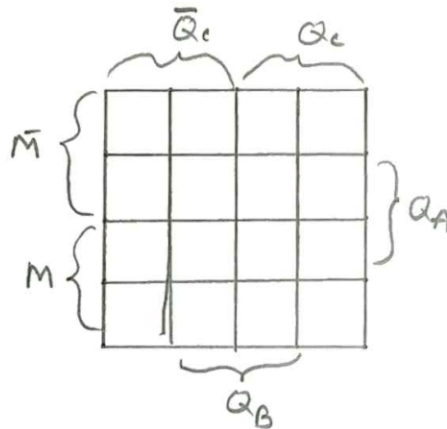Boolean Expression :

$$T_B = M \oplus Q_B$$

$$T_C = \bar{M}Q_CQ_B + M\bar{Q}_B\bar{Q}_C$$

Circuit Diagram:


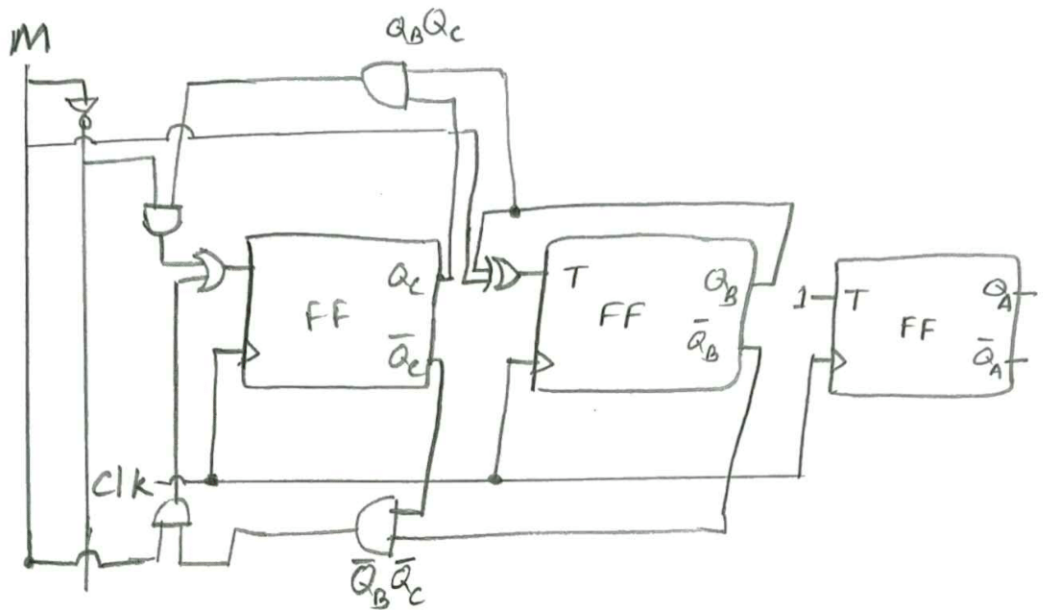


Fig: 3-bit up-down counter

State Diagram:

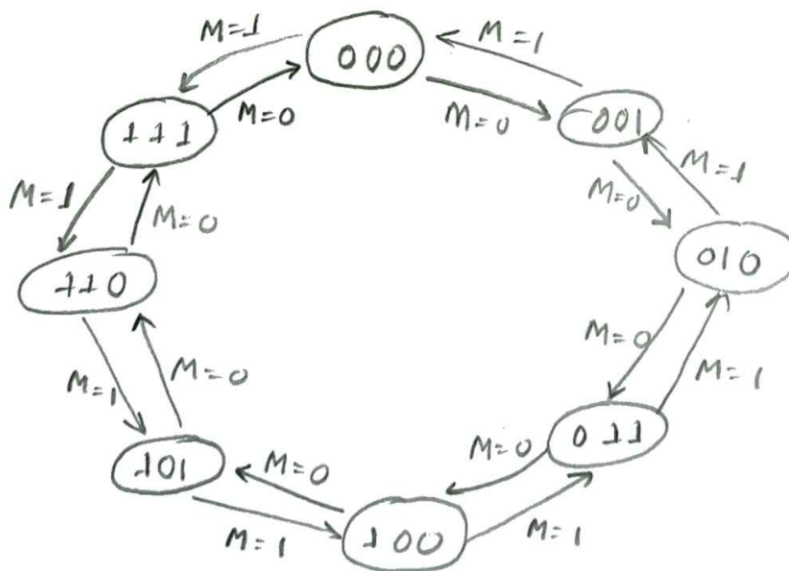

Mode, $M=0$; \uparrow up count
 Mode, $M=1$; \downarrow down count