

## Objective:

- ① To design a register file that is 16-bit wide. Label properly the inputs/outputs/selection.
- ② To design the interfacing for reading data from any of those registers.
- ③ To design the interfacing for writing data to any of those registers. make sure it has the write control signal.

## Equipments:

- ① Logisim software.

## Block Diagram

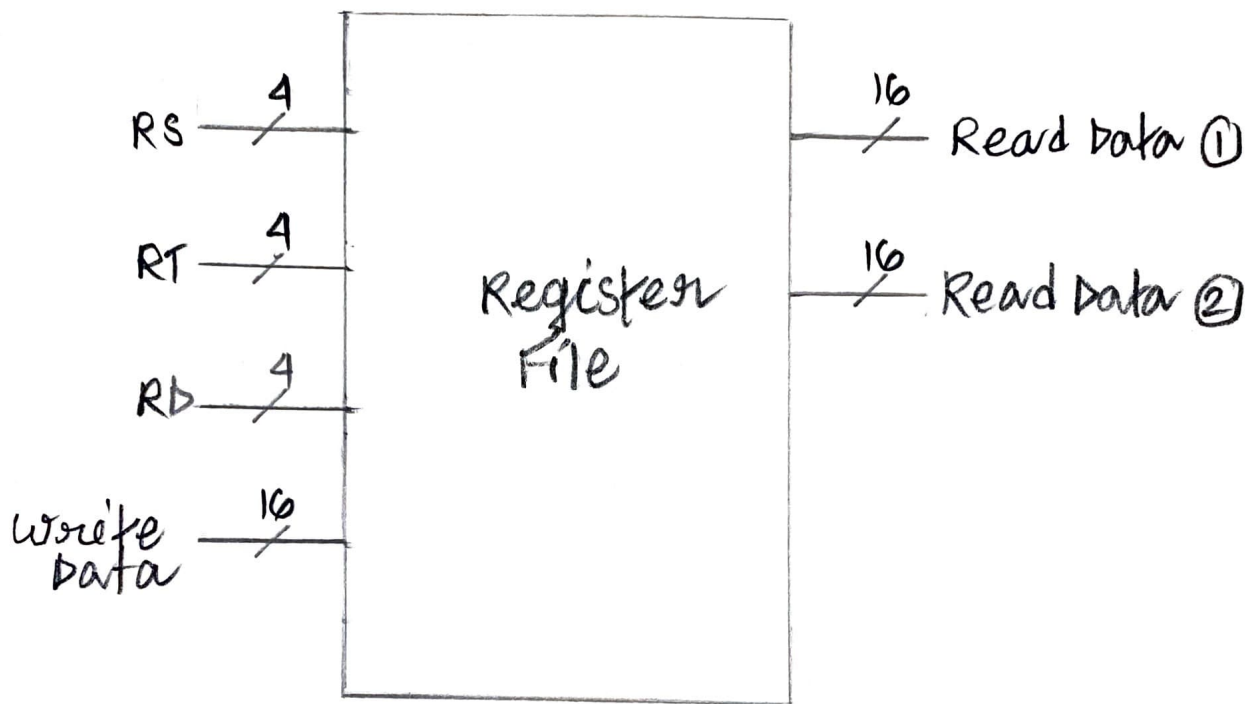


Fig: A 16-bit Register File

## Circuit Diagram:

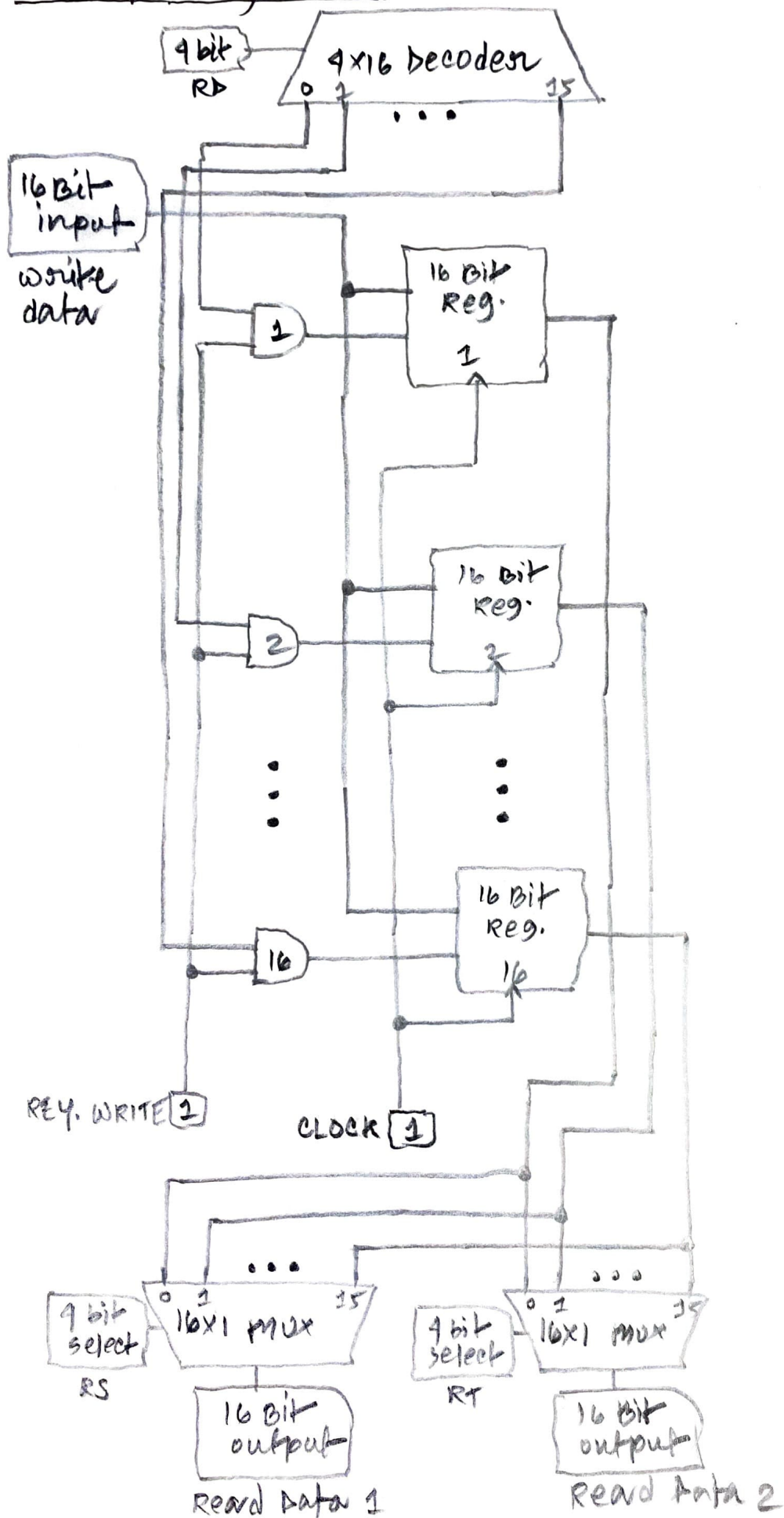


Fig: 16-bit Register File

## Discussion:

In this experiment, we needed to design a 16-bit wide register file. For the 16-bit register we were given,  $RS$  (source register 1) =  $RT$  (source register 2) =  $RD$  (destination register) = 4-bits. We needed 4x16 decoder for writing data in one register and we needed 2 muxs (16x1 each) for reading data from two registers. We built the whole circuit in logisim by connecting all the wires carefully from decoder to registers to mux.

This was a pretty easy task to do as there was no hardware implementation so we built the circuit without any error and got the expected output.